

# Ü5: Kombinatorische und sequentielle Automatenmodelle in VHDL


## Aufgabe 1:

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY aufgabe_eins IS
    PORT(B, C, D : IN std_logic;
         A_OUT, E : OUT std_logic);
END aufgabe_eins;

ARCHITECTURE aufgabe_eins_arch OF aufgabe_eins IS
    signal A : std_logic;
BEGIN
    P1 :process (B, C, D)
        BEGIN
            A_OUT <= B or C and D
            A <= B or C and D
        end process P1;

     P2 :process (A,C)
        BEGIN
            E <= A and not C
        end process P2;
END aufgabe_eins_arch;
```



## Aufgabe 2:

- UND-Gatter
- 1-Pegel gesteuertes D-Flip-Flop

# Ü5: Kombinatorische und sequentielle Automatenmodelle in VHDL

## Aufgabe 3:

### Vorderflankengesteuertes D-Flip-Flop

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY dff IS
    PORT(D, CLK : IN std_logic;           -- D und Clock Signale
         Q,Q_not: OUT std_logic);       -- Q und Q_not Ausgangs-Signale
END dff;

ARCHITECTURE dff_arch OF dff IS
BEGIN
    process (CLK)
    BEGIN
        if (CLK'event and CLK = '1') then
            Q <= D;
            Q_not <= not D;
        end if;
    end process;
END dff_arch;
```

# Ü5: Kombinatorische und sequentielle Automatenmodelle in VHDL

## Aufgabe 4:

### Teil a) Vorderflankengesteuertes D-Flip-Flop mit asynchronem Reset:

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY dff IS
    PORT(D,CLK, RESET : IN std_logic;
         Q,Q_not: OUT std_logic);
END dff;

ARCHITECTURE dff_arch OF dff IS
BEGIN
    process(CLK, RESET)
    begin
        if (RESET='1') then
            Q <= '0';
            Q_not <= '1';
        elsif (CLK'event and CLK='1') then
            Q <= D;
            Q_not <= not D;
        end if;
    end process;
END dff_arch;
```

### Teil b) Vorderflankengesteuertes D-Flip-Flop mit synchronem Reset:

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY dff IS
    PORT(D,CLK, RESET : IN std_logic;
         Q,Q_not: OUT std_logic);
END dff;

ARCHITECTURE dff_arch OF dff IS
BEGIN
    process(CLK)
    begin
        if (CLK'event and CLK = '1') then
            if (RESET = '1') then
                Q <= '0';
                Q_not <= '1';
            else
                Q <= D;
                Q_not <= not D;
            end if;
        end if;
    end process;
END dff_arch;
```

# Ü5: Kombinatorische und sequentielle Automatenmodelle in VHDL

## Aufgabe 5:

Teil a) **VHDL-Prozeß-Modell in Huffman-Normalform für den gegebenen endlichen Automaten:**

```
entity FSM is
    port (CLK,RESET, X: in bit;
          Y1,Y2: out bit);
end FSM;

architecture BEH_2PR of FSM is
    type STATE is (S0, S1, S2);
    signal CURRENT_STATE, NEXT_STATE: STATE;

begin
    SEQ: process (CURRENT_STATE, X)
    begin
        case CURRENT_STATE is
            when S0 =>
                if (X = '0') then
                    NEXT_STATE <= S0;
                    Y1 <= '0'; Y2 <= '1';
                else
                    NEXT_STATE <= S1;
                    Y1 <= '1'; Y2 <= '0';
                end if;
            when S1 =>
                if X = '1' then
                    NEXT_STATE <= S2;
                    Y1 <= '0'; Y2 <= '0';
                else
                    NEXT_STATE <= S1;
                    Y1 <= '1'; Y2 <= '0';
                end if;
            when S2 =>
                if X = '1' then
                    NEXT_STATE <= S0;
                    Y1 <= '0'; Y2 <= '0';
                else
                    NEXT_STATE <= S1;
                    Y1 <= '1'; Y2 <= '1';
                end if;
        end case;
    end process;

    -- process to hold synchronous elements
    MEM: process (CLK,RESET)
    begin
        if RESET then
            CURRENT_STATE <= S0;
        elsif CLK'event and CLK = '1' then
            CURRENT_STATE <= NEXT_STATE;
        end if;
    end process;
end BEH_2PR;
```

# Ü5: Kombinatorische und sequentielle Automatenmodelle in VHDL

## Teil b) Änderung für einen asynchronen Automaten:

```

...
-- process to hold synchronous elements
MEM: process (NEXT_STATE,RESET)
begin
    if RESET then
        CURRENT_STATE <= S0;
        NEXT_STATE <= S0;
    else
        CURRENT_STATE <= NEXT_STATE;
    end if;
end process;
...

```

## Teil c) Ausgabe, wenn X dauerhaft auf '1' gesetzt wird:

Y1 = 100100100 ...  
Y2 = 000000000 ...

## Teil d) Berechnung des Automaten bei gegebener X-Folge und einem Takt von 5ns:

t [ns]	0	2	5	8	10	11	12	13	15	16	20	25	30
X	0	1	1	1	1	0	1	0	0	1	1	1	1
Y1	u	1	0	0	0	1	0	1	1	0	0	1	0
Y2	u	0	0	0	0	1	0	1	0	0	0	0	0
NS	u	S1	S2	S2	S0	S1	S0	S1	S1	S2	S0	S1	S2
CS	S0	S0	S1	S1	S2	S2	S2	S2	S1	S1	S2	S0	S1